

Due: 11:59 pm on Nov 6, 2024

## Problem 1

## Part A

Prove the equation given in class:

$$\mathbf{F} = \frac{d\mathbf{p}}{dt} = q(\mathbf{E} + \mathbf{V} \times \mathbf{B}) = q\left[-\nabla V - \frac{\partial \mathbf{A}}{\partial t} + \mathbf{V} \times (\nabla \times \mathbf{A})\right]$$

## Part B

Check that the vector potential  $\mathbf{A}$  defined in two different ways as

1.  $\mathbf{A}(\mathbf{r}) = \frac{1}{2}(\mathbf{B} \times \mathbf{r})$ , with  $\mathbf{B} = B\hat{n}_z$ ;
2.  $\mathbf{A}(\mathbf{r}) = xB\hat{n}_y$ , called the Landau gauge, with uniform magnetic field of magnitude  $B$  in the  $z$ -axis direction.

Also check that in both cases  $\text{div}\mathbf{A} = 0$ , *i.e.* in both are some particular realizations of the Coulomb gauge.

## Problem 2

## Part A | Optional

Consider two light bulbs connected in series around a solenoid producing a sinusoidally varying magnetic field. If we alter the circuit by connecting a thick copper wire across the circuit, we find that the top bulb gets much brighter and the bottom one no longer glows. Why does this happen?

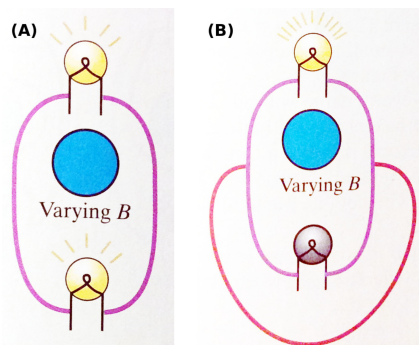


Figure 1: 2A

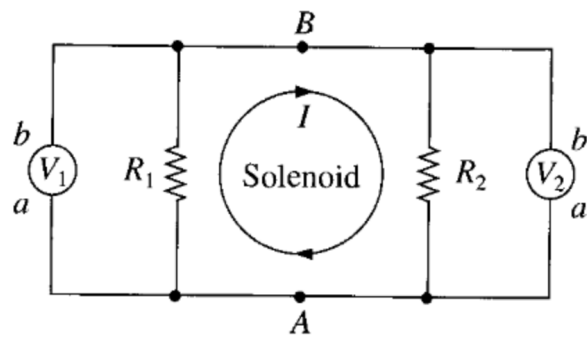


Figure 2: 2B

## Part B

The current in a long solenoid piercing the plane of the circuit is increasing linearly with time, so that the magnetic flux through the cross-section of the solenoid  $\Phi_B = \alpha t$ . Two voltmeters are connected to diametrically opposite points  $A$  and  $B$ , together with resistors  $R_1$  and  $R_2$ .

Show that the readings on voltmeters are  $V_1 = \frac{\alpha R_1}{R_1 + R_2}$  and  $V_2 = -\frac{\alpha R_2}{R_1 + R_2}$ , respectively, *i.e.*  $V_1 \neq V_2$ , even though they are connected to the same points.

Assume that these are ideal voltmeters that draw negligible current (huge resistance), and that a voltmeter registers  $\int_a^b \mathbf{E} \circ d\mathbf{l}$  between the terminals and through the meter.

## Problem 3

## Part A

Two coils are wrapped around each other. The current travels in the same sense around each coil. One coil has self-inductance  $L_1$ , and the other coil has self-inductance  $L_2$ . The mutual inductance of the two coils is  $M$ . Show that if the two coils are connected in parallel, the equivalent inductance of the combination is  $L = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$ .

## Part B

A transformer takes an input AC voltage of amplitude  $V_1$ , and delivers an output voltage of amplitude  $V_2$ , which is determined by the turns ratio,  $V_2/V_1 = N_2/N_1$ . If  $N_2 > N_1$  the output voltage is greater than the input voltage. Why doesn't this violate conservation of energy? *Answer:* Power is the product of voltage and current; evidently if the voltage goes up, the current must come down.

The purpose of this problem is to see exactly how this works out, in a simplified model.

1. In an ideal transformer the same flux passes through all turns of the primary and of the secondary. Show that in this case  $M^2 = L_1 L_2$ , where  $M$  is the mutual inductance of the coils and  $L_1, L_2$  are their individual self-inductance.
2. Suppose the primary is driven with AC voltage  $V_{\text{in}} = V_1 \cos \omega t$ , and the secondary connected to a resistor with resistance  $R$ . Show that the two currents satisfy the relations

$$L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = V_1 \cos \omega t, \quad L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = -I_2 R.$$

3. Using the result in (a) solve the equations for  $I_1$  and  $I_2$ . (Assume that  $I_1$  has no DC component.)
4. Show that the output voltage  $V_{\text{out}} = I_2 R$  divided by the input voltage  $V_{\text{in}}$  is equal to the turns ratio, *i.e.*  $V_{\text{out}}/V_{\text{in}} = N_2/N_1$ .
5. Calculate the input power  $P_{\text{in}} = V_{\text{in}} I_1$  and the output power  $P_{\text{out}} = V_{\text{out}} I_2$ , and show that their averages over a full cycle are equal.

## Part C

One application of  $LRC$  series circuits is to high-pass or low-pass filters, which filter out either the low- or high-frequency components of a signal.

1. In a high-pass filter the output voltage is taken across the  $LR$  combination. Derive an expression for  $V_{hi}/V_s$ , the ratio of the output and source amplitudes as a function of the angular frequency  $\omega$  of the source. Show that when  $\omega$  is small, this ratio is proportional to  $\omega$  and thus is small, and show that the ratio approaches unity in the limit of large frequency.
2. In a low-pass filter the output voltage is taken across the capacitor in an  $LRC$  circuit. Derive an expression for  $V_{lo}/V_s$ , the ratio of the output and source amplitudes as a function of the angular frequency  $\omega$  of the source. Show that when  $\omega$  is large this ratio is proportional to  $\omega^{-2}$  and thus is small, and show that the ratio approaches unity in the limit of small frequency.

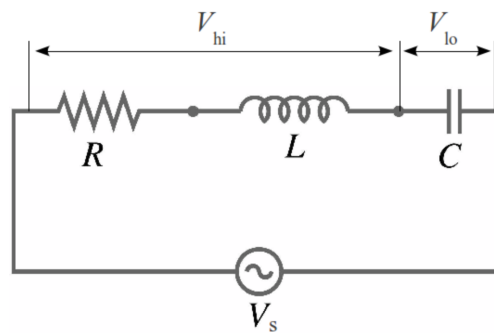


Figure 3: 3C